

Implementation of an 8-bit Microprocessor and Signal Monitoring System

Pranav Kumar (13490)
Supervised by: Dr. S. Qureshi

IIT Kanpur

November 9, 2016

Outline I

- ① Introduction
- ② Motivation and Relevance
- ③ Part I - Microprocessor Implementation
 - Introduction
 - Instruction Set Architecture
 - Datapath
 - Memory
 - Bits of the Control Word
- ④ Part I - Microprocessor Results
- ⑤ Part II - Signal Monitoring System Implementation - XADC Functionality
 - Introduction
 - XADC Description
 - XADC Operating Modes and Input Signal Types
 - Status and Control Registers
 - Instantiating and initializing the XADC

Outline II

6 Part II - Signal Monitoring System Results

7 Future Work

8 References

- Embedded microprocessors, today, are used in a variety of electronic products.
- The Central Processing Unit is the core of the computer.
- In Part I of this project, I have implemented an FPGA-based 8-bit microprocessor which does basic 8085-level ALU and memory operations.
- It is designed in Verilog and mainly consists of 8 8-bit registers in a Register File, 256-word memory with 16-bit words, a Control Unit and a Function Unit implementing ALU operations.

- An Analog-to-Digital Converter is of prime importance whenever real-world signals come into play.
- This is used in the second part, where a custom microprocessor is realized.
- The XADC (Analog-to-Digital Converter) is interfaced to convert an incoming real-world analog signal to digital form. This data is validated and further checked to determine if it is noise or contains a signal.

Motivation and Relevance

- The 8085 is regarded as the father of all CPU designs and all later microprocessors were an enhancement of it.
- Thus, I would gain a good idea about basic computer architecture by implementing the same from scratch.
- Part II of this project (Signal Monitoring System) has great applications in the monitoring of illicit activities in forests.
- Forests are troubled by the increase of deforestation and poaching of endangered wildlife.
- For that, an ASIC based on my FPGA-prototype of an Audio (Analog Signal) Monitoring System will help in surveillance. The chip will detect any out-of-the-ordinary sounds in the surroundings and communicate a warning to the base station.

Part I - Microprocessor Implementation

- Microprocessors are the devices in a computer that make things happen.
- An 8-bit microprocessor can read/write 1 byte at a time and can directly access 256 bytes.
- In this part, I implement a general purpose RISC (reduced instruction set computing) microprocessor with a clock rate of 50 MHz (on-board oscillator).
- The implementation is done in a modular fashion and the descriptions of the various modules follow.

Instruction Set Architecture

The processor is designed to input 16-bit set of instructions. The format is as follows.

| | | | | | | |
|-------------|----|----|----|-------|-------|-------|
| 15 14 13 12 | 11 | 10 | 9 | 8 7 6 | 5 4 3 | 2 1 0 |
| FS | MD | RW | MB | DA | AA | BA |

Here AA, BA and DA are the A, B and Destination addresses i.e. one register out of R0 to R7. The control word further contains MB (Mux B select), FS (Function select), MD (Mux D select) and RW (Register Write). The control word is held by the Instruction Register module and fed into the datapath.

Datapath

Datapath is a set of functional units that carry out data processing operations. It is comprised of a register file, a function unit and two multiplexers.

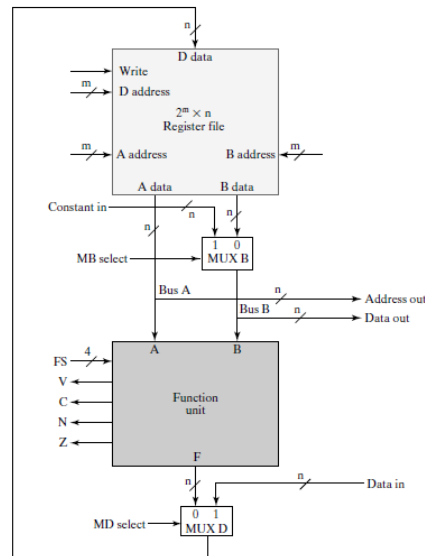


Figure 1: The Datapath

Register File

A simpler 4-register Register File with n -bit data storage is shown in figure 2.

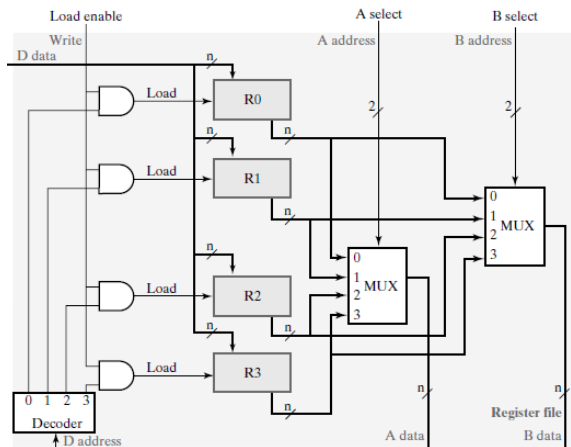


Figure 2: A simple $4 \times n$ register file

The operands for and the result of ALU operations is stored in the registers in the register file and could be re-used in a subsequent operation or saved into memory.

Function Select Bits

| Function Select | Operation | Function |
|-----------------|-------------------------|---------------------------|
| 0000 | $F = A$ | Transfer A |
| 0001 | $F = A + 1$ | Increment A |
| 0010 | $F = A + B$ | Addition |
| 0011 | $F = A + B + 1$ | Add with carry input of 1 |
| 0100 | $F = A + \tilde{B}$ | A plus 1s complement of B |
| 0101 | $F = A + \tilde{B} + 1$ | Subtraction |
| 0110 | $F = A - 1$ | Decrement A |
| 0111 | $F = A$ | Transfer A |
| 1000 | $F = A \text{ AND } B$ | AND |
| 1001 | $F = A \text{ OR } B$ | OR |
| 1010 | $F = A \text{ XOR } B$ | XOR |
| 1011 | $F = \tilde{A}$ | NOT |
| 1100 | $F = B$ | Transfer B |
| 1101 | $F = B >> 1$ | Right Shift by 1 |
| 111X | $F = B << 1$ | Left shift by 1 |

Memory

The memory has 256 words and each word is comprised of 16 bits. An 8-bit address specifies the memory location which is being written to or read from.

 


Figure 3: Memory

Bits of the control word

The function of various bits in the Control Word are as follows.

| AA, BA, DA | Register select |
|------------|-----------------|
| 000 | Select R0 |
| 001 | Select R1 |
| 010 | Select R2 |
| 011 | Select R3 |
| 100 | Select R4 |
| 101 | Select R5 |
| 110 | Select R7 |
| 111 | Select R7 |

Table 2: AA, BA and DA bits

| MD | Operation |
|----|--|
| 0 | Bus D is fed with the ALU output |
| 1 | Bus D is fed with an external data input |

Table 3: Mux D select bit

| MB | Operation |
|----|--|
| 0 | BDATA from the register file is fed into the ALU |
| 1 | An external data input is fed into the ALU |

Table 4: Mux B select bit

| RW | Operation |
|----|----------------------|
| 0 | No writing to memory |
| 1 | Writing to memory |

Table 5: RW bit

The operations of the Function Select (FS) bits have already been tabulated in Table 1.

Part I - Microprocessor Results

The code is provided in Appendix A of the report and the results follow. The testbenches for the codes are given at home.iitk.ac.in/~pranavk/ugp3/tbs

- Multiplexer

 


Figure 4: Multiplexer Results

- Decoder

 


Figure 5: Decoder Results

- Register

 


Figure 6: Register Results

- Register File

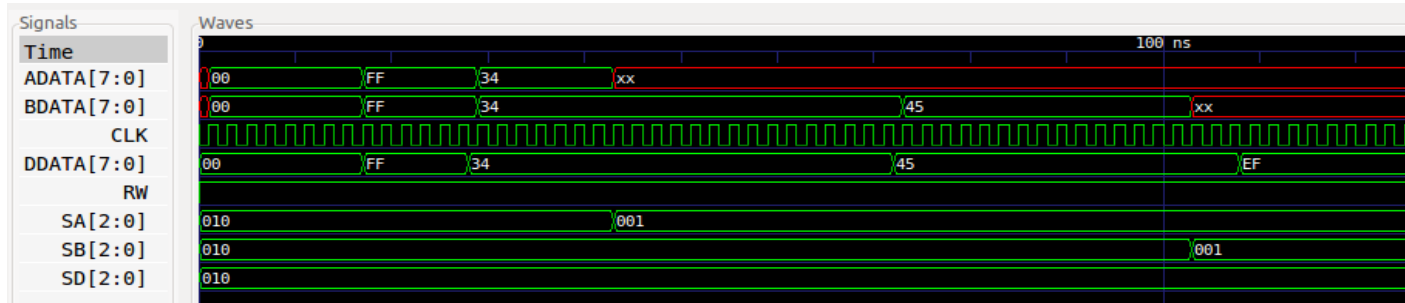


Figure 7: Register File Results

- Memory

 


Figure 8: Memory Results

● Microprocessor

 


Figure 9: Microprocessor Results - I

 


Figure 10: Microprocessor Results - II

Part II - Signal Monitoring System Implementation - XADC Functionality

- This part of the project makes use of an XADC (Analog-to-Digital Converter) on the Basys3 FPGA Board to firstly digitize an incoming analog signal.
- Further, it is checked if the signal is deterministic or random noise.
- If it is deterministic, an alarm is raised for an indefinite time until it is reset manually.

XADC Description

- The XADC includes a dual channel 12-bit, 1 Mega sample per second (MSPS) ADC and on-chip sensors.
- The dual ADCs support a range of operating modes and various analog input signal types.

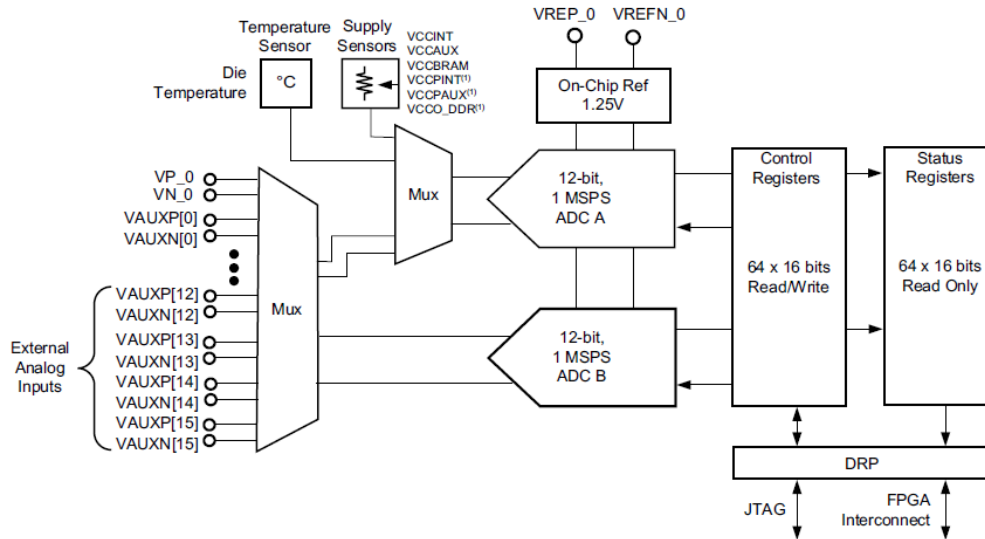


Figure 11: XADC Block Diagram

XADC Operating Modes and Input Signal Types

The XADC includes several operating modes like -

- default
- Single Channel Mode
- Simultaneous Sampling Mode.

The external analog input channels can be configured to operate in unipolar or bipolar mode -

- Unipolar Mode - Input range to the ADC is 0V to 1V. The ADC produces 000h when 0V is present and FFFh when 1V is present on the input.
- Bipolar Mode - Input range is -0.5V to 0.5V in this mode. The ADC produces a two's complement output code, that is, 000h for 0V, 7FFh for 0.5V and 800h for -0.5V.

As I am dealing with real-world signals, I'll be operating in the bipolar mode.

Status Registers

The status registers contain the results of an analog-to-digital conversion of the on-chip sensors and external analog channels. Each such measurement is mapped to a unique address.

| Name | Address | Measurements of |
|---------------|------------|----------------------------|
| Temperature | 00h | On-chip temperature sensor |
| VCCINT | 01h | Power Supply Sensor |
| VCCAUX | 02h | Power Supply Sensor |
| VCCBRAM | 06h | Power Supply Sensor |
| VP/VN | 03h | Dedicated analog input |
| VAUXP/N[15:0] | 10h to 1Fh | External analog inputs |

Table 6: Status Registers (Read-Only)

Control Registers

These registers are used to configure the XADC operation.

| Name | Address | Software Attribute | Description |
|---------------|---------|--------------------|-----------------------|
| Config Reg 0 | 40h | INIT40 | To configure XADC |
| Config Reg 1 | 41h | INIT41 | To configure XADC |
| Config Reg 2 | 42h | INIT42 | To configure XADC |
| Test Regs 0-4 | 43h-47h | INIT43-INIT47 | Default value = 0000h |

Table 7: XADC Control Registers

Instantiating and initializing the XADC

- To allow access to the status registers, the XADC must be instantiated. This refers to initialization of the control registers.
- Once the XADC has been instantiated, the different ports of it can be made use of.

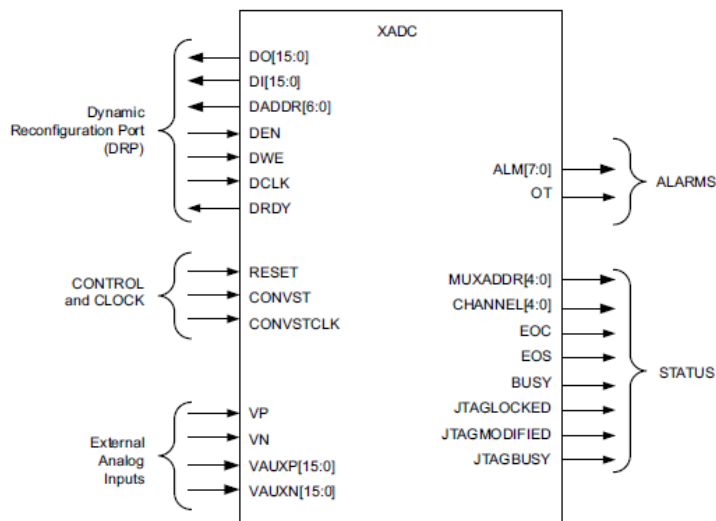


Figure 12: XADC Ports

The table below lists the functionality of the used ports.

| Port | I/O | Description |
|---------------|---------|-------------------------------------|
| DI[15:0] | Inputs | Input data bus |
| DO[15:0] | Outputs | Output data bus |
| DADDR[6:0] | Input | Address bus |
| DEN | Input | Enable signal |
| DWE | Input | Write enable signal |
| DCLK | Input | Clock input for the DRP = 50MHz |
| DRDY | Output | Data ready signal for the DRP |
| RESET | Input | Asynchronous ADC Reset signal |
| CONVST | Input | Convert Start Input |
| CONVSTCLK | Input | Convert Start Clock Input |
| VP, VN | Input | Dedicated Analog Input Pair |
| VAUXP/N[15:0] | Inputs | Sixteen external analog input pairs |
| EOC | Output | End of conversion signal |
| EOS | Output | End of sequence signal |
| Busy | Output | ADC Busy signal |

Table 8: XADC Port Descriptions

- The external input is averaged over 32 samples so as to reduce the error. On averaging over N samples, the standard deviation of the error reduces to one- \sqrt{N} th of the original.
- Once error is reduced, the averaged digitized value is checked with a threshold (0.1V).
- If it is above it, I claim it to be a deterministic signal and raise an indefinite alarm.
- The second analog signal is the external Reset signal. If it goes above a certain value (0.5V), the alarm is reset.

Part II - Signal Monitoring System Results

| TIME | VAUXP[0] | VAUXN[0] | VAUXP[1] | VAUXN[1] |
|--------|----------|----------|----------|----------|
| 00000 | 0.000 | 0.0 | 0.1 | 0.0 |
| 50000 | 0.2 | 0.0 | 0.0 | 0.0 |
| 90000 | 0.5 | 0.0 | 0.0 | 0.0 |
| 121000 | 0.0 | 0.0 | 0.6 | 0.0 |

Table 9: Input 1

 


Figure 13: Results 1

The ALARM bit is set whenever the average of the last 32 samples of MEASUREDAUX0 goes above 0.1V and is reset whenever the average of the last 32 samples of MEASUREDAUX1 goes above 0.5V.

| TIME | VAUXP[0] | VAUXN[0] | VAUXP[1] | VAUXN[1] |
|--------|----------|----------|----------|----------|
| 00000 | 0.000 | 0.0 | 0.1 | 0.0 |
| 10000 | 0.1 | 0 | 0.15 | 0 |
| 20000 | 0.15 | 0 | 0.1 | 0 |
| 30000 | 0.13 | 0 | 0.65 | 0 |
| 40000 | 0.08 | 0 | 0.15 | 0 |
| 50000 | 0.2 | 0.0 | 0.0 | 0.0 |
| 60000 | 0.3 | 0 | 0.15 | 0 |
| 65000 | 0.35 | 0 | 0.15 | 0 |
| 70000 | 0.1 | 0 | 0.15 | 0 |
| 80000 | 0 | 0 | 0.15 | 0 |
| 85000 | 0.05 | 0 | 0.65 | 0 |
| 90000 | 0.5 | 0.0 | 0.0 | 0.0 |
| 100000 | 0.0 | 0 | 0.15 | 0 |
| 110000 | 0.5 | 0 | 0.15 | 0 |
| 121000 | 0.0 | 0.0 | 0.6 | 0.0 |

Table 10: Input 2

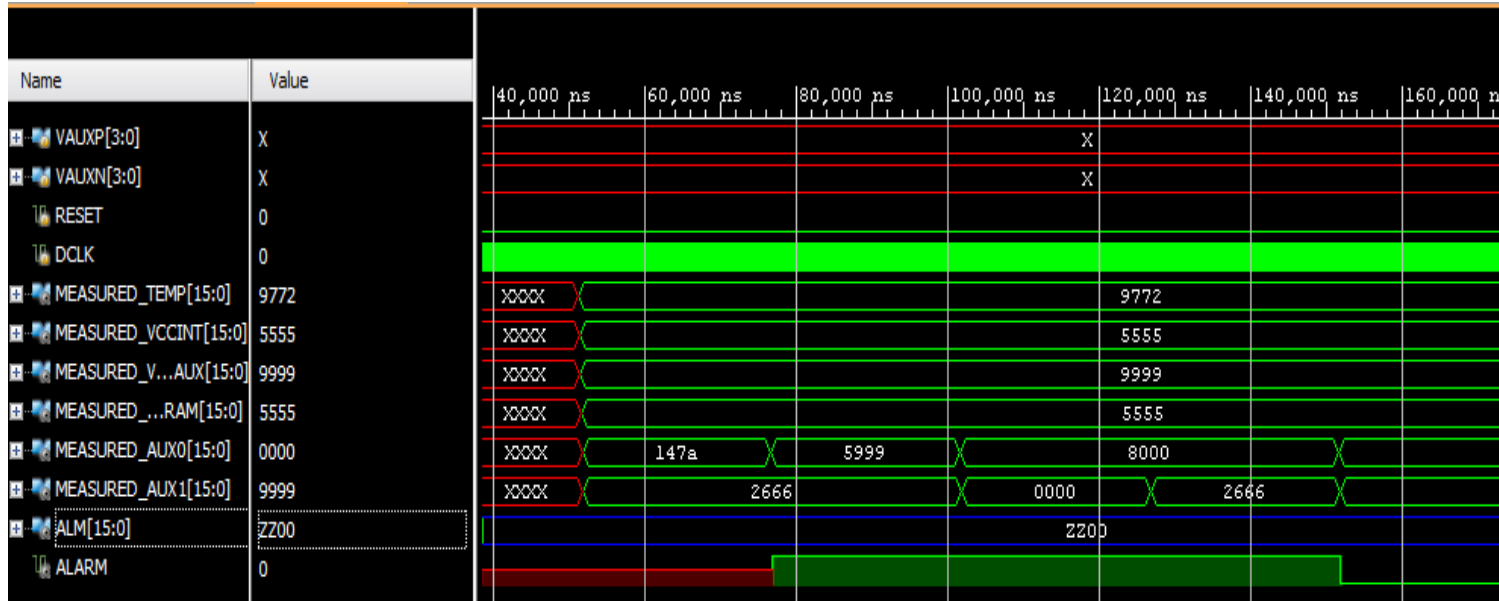







Figure 14: Results 2

The averaging is evident in Result 2 as the measured value doesn't change every 10000 ns as in the analog stimulus file, rather it changes every 32 samples (= 32000 ns) to a value equal to the average of the previous 32 samples.

- The Signal Monitoring System can be extended and built as a System-on-chip for forest surveillance purposes.
- It would efficiently determine any out-of-the-ordinary sounds (analog signals) in the forest and any anomalous situation would be immediately reported to the base station via an alarm.
- Once the situation has been checked on and resolved, the alarm may be stopped by an external electromagnetic reset signal to the ASIC.

References

-  Xilinx. 7 Series FPGAs and Zynq-7000 All Programmable SoC XADC Dual 12-Bit 1 MSPS Analog-to-Digital Converter User Guide. <http://www.xilinx.com>. UG480 (v1.9) September 27, 2016
-  Y.S.Chauhan. Memory Design and Register Transfer, Micro-operations.[PDF Document] Digital Electronics(EE370). IIT Kanpur.2015.
-  E. Ayeh, Y. Morita, K. Agbedanu, O. B. Adamo, and P. Guturu. FPGA Implementation of an 8-bit Simple Processor. In Proceedings of the IEEE Region 5 Technical, Professional and Student Conference (TPS), pp. 1-5, 2008.
-  Xilinx. Spartan-3E FPGA Starter Kit Board User Guide. UG230 (v1.2). <http://www.xilinx.com>. January 20, 2011
-  M. Morris Mano, Charles R. Kime. Logic and Computer Design Fundamentals. Pearson. 2004. ISBN-13: 9780131405394